

Gmin stepping succeeded in finding the operating point.


Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---


Name:	m5	m4	m3	m2	m1
Model:	cmosp	cmosp	cmosp	cmosn	cmosn
Id:	-5.27e-05	-2.44e-05	-2.44e-05	2.44e-05	2.44e-05
Vgs:	-1.00e+00	-9.74e-01	-9.74e-01	5.84e-01	5.84e-01
Vds:	-9.01e-01	-1.00e+00	-9.74e-01	4.84e-01	5.10e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	-3.16e-01	-3.16e-01
Vth:	-4.18e-01	-4.17e-01	-4.17e-01	5.00e-01	5.00e-01
Vdsat:	-4.38e-01	-4.17e-01	-4.17e-01	8.86e-02	8.85e-02
Gm:	1.63e-04	7.94e-05	7.93e-05	4.20e-04	4.20e-04
Gds:	2.39e-06	1.00e-06	1.02e-06	2.99e-06	2.93e-06
Gmb:	5.34e-05	2.57e-05	2.56e-05	1.06e-04	1.06e-04
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	3.78e-15	1.89e-15	1.89e-15	1.79e-14	1.79e-14
Cgdov:	3.78e-15	1.89e-15	1.89e-15	1.79e-14	1.79e-14
Cgbov:	9.41e-19	9.41e-19	9.41e-19	9.66e-19	9.66e-19
dQgdVgb:	4.66e-14	2.33e-14	2.33e-14	1.73e-13	1.73e-13
dQgdVdb:	-3.72e-15	-1.86e-15	-1.86e-15	-1.75e-14	-1.75e-14
dQgdVsb:	-4.22e-14	-2.11e-14	-2.11e-14	-1.44e-13	-1.44e-13
dQddVgb:	-1.95e-14	-9.76e-15	-9.76e-15	-7.22e-14	-7.22e-14

Name:	m6	m0	mref
Model:	cmosn	cmosn	cmosn
Id:	5.27e-05	4.87e-05	5.00e-06
Vgs:	4.56e-01	4.56e-01	4.56e-01
Vds:	8.99e-01	3.16e-01	4.56e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00
Vth:	4.06e-01	4.09e-01	4.08e-01
Vdsat:	6.57e-02	6.46e-02	6.48e-02
Gm:	1.05e-03	9.86e-04	1.01e-04
Gds:	6.47e-06	8.16e-06	7.06e-07
Gmb:	3.05e-04	2.86e-04	2.92e-05
Cbd:	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00
Cgsov:	8.23e-14	8.23e-14	8.23e-15
Cgdov:	8.23e-14	8.23e-14	8.23e-15
Cgbov:	9.66e-19	9.66e-19	9.66e-19
dQgdVgb:	7.48e-13	7.44e-13	7.45e-14
dQgdVdb:	-8.06e-14	-8.10e-14	-8.07e-15
dQgdVsb:	-5.92e-13	-5.85e-13	-5.87e-14
dQddVgb:	-3.00e-13	-2.97e-13	-2.98e-14
dQddVdb:	8.13e-14	8.17e-14	8.15e-15
dQddVsb:	2.88e-13	2.84e-13	2.85e-14
dQbdVgb:	-1.49e-13	-1.49e-13	-1.50e-14
dQbdVdb:	2.16e-16	-1.28e-16	1.08e-17

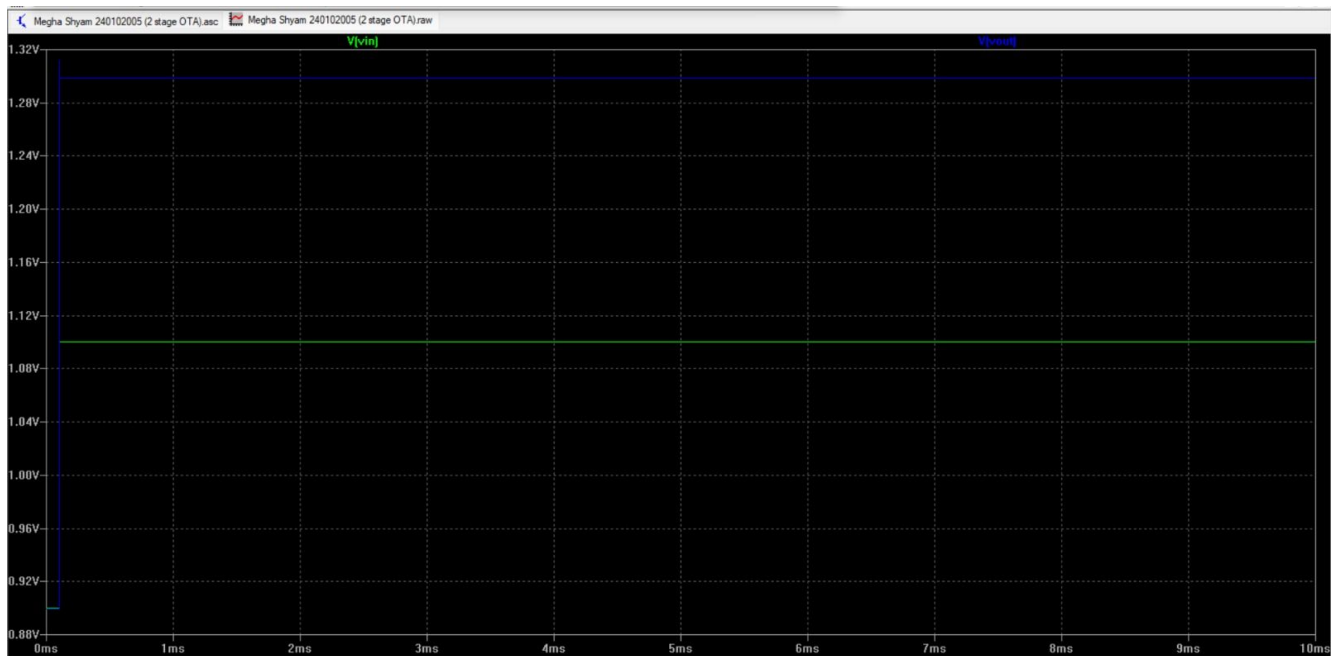Transient response of the closed loop amplifier with a 0.2v step input.



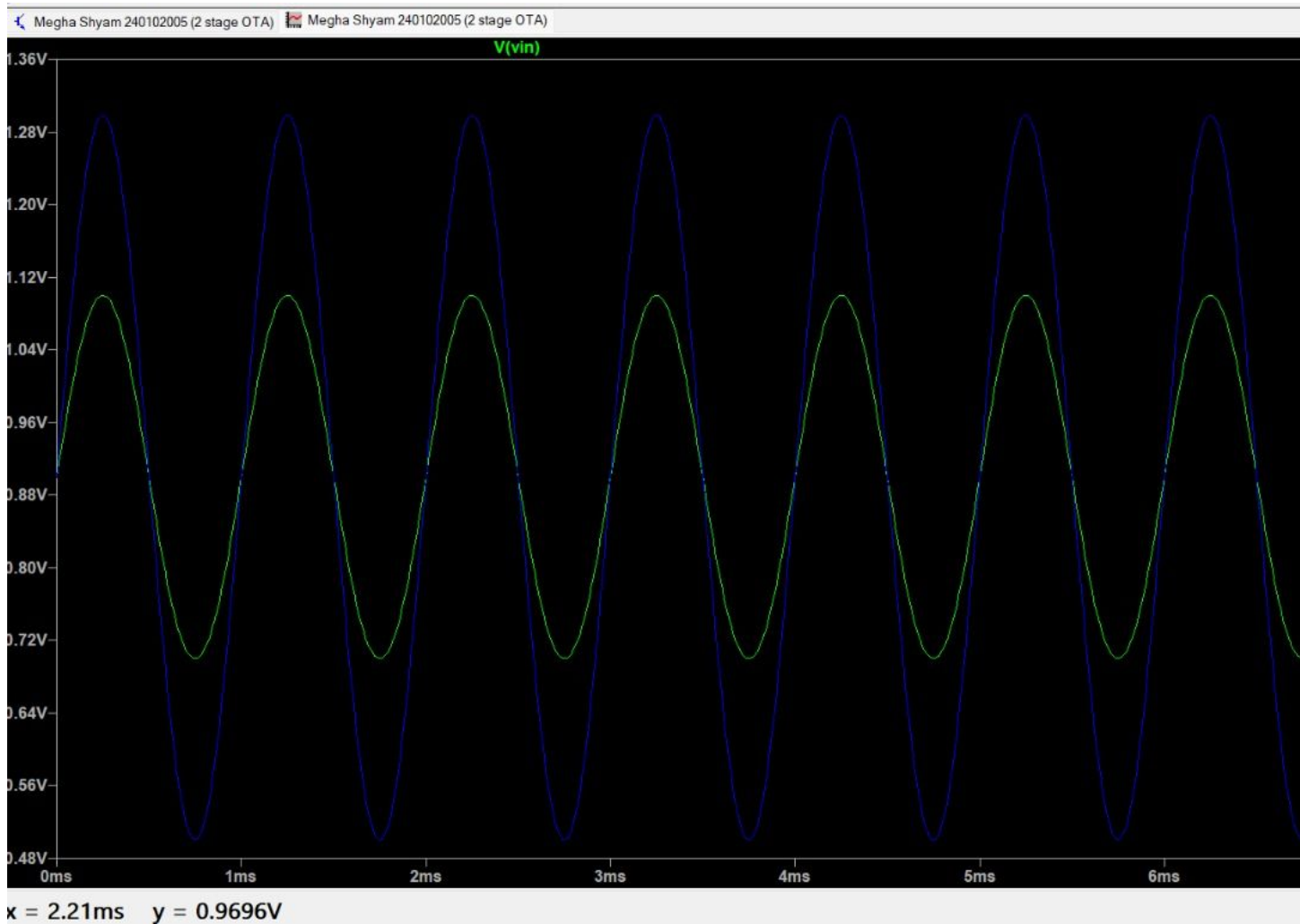Response of the closed loop amplifier with a 0.2v sinusoidal input.



Frequency Response of the system

